



The sense resistor was sized at 0.04 ohms. This would allow for a max voltage of 0.1 volts. This will give us enough resolution on the ADC for effective current sensing. A 10uF and two 1uF capacitors are used on the 3.3V line for voltage smoothing and for the various LEDs powered by the rail.

Sheet: /
File: motor_driver.sch

Title: Motor Driver Board – Cole Mortensen, u0998038 – ECE 5780–001

Size: USLetter Date:
KiCad E.D.A. kicad 4.0.7

Rev:
Id: 1/1